

Example 62: Traffic Lights

It is often useful to be able to sequence through an arbitrary number of states, staying in each state an arbitrary amount of time. For example, consider the set of traffic lights shown in Figure 8.13. The lights are assumed to be at a four-way intersection with one street going north-south and the other road going east-west.

 


Figure 8.13 Six colored LEDs can represent a set of traffic lights

To simulate these traffic lights we will use the red, yellow, and green LEDs connected to $ld[7:2]$ on the BASYS board and cycle through the six states shown in Table 8.2. A state diagram for controlling these traffic lights is shown in Fig. 8.14. If we use a 3 Hz clock to drive this state diagram then a delay of 1 second is achieved by staying in a state for three clock cycles. Similarly, a delay of 5 second is achieved by staying in a state for fifteen clock cycles. The *count* variable in Fig. 8.14 will be reset to zero when moving to the next state after a timeout.

Listing 8.6 is a Verilog program that implements the state diagram in Fig. 8.14 and its simulation is shown in Fig. 8.15. Because we need a counter for the delay count it is more convenient in this case to combine the state register and combinational modules C1 in the Moore machine in Fig. 8.3 into a single sequential *always* block as shown in Listing 8.6. Note in this case we use only a single *state* variable.

To generate the 3 Hz signal we will use the version of *clkdiv* shown in Listing 8.7. The top-level Verilog program is given in Listing 8.8.

Table 8.2 Traffic Light States

State	North - South	East - West	Delay (sec.)
0	Green	Red	5
1	Yellow	Red	1
2	Red	Red	1
3	Red	Green	5
4	Red	Yellow	1
5	Red	Red	1

 


Figure 8.14 State diagram for controlling traffic lights

 


Figure 8.15 Simulation of the Verilog program in Listing 8.4

Listing 8.6 traffic.v

```
// Example 62a: traffic lights
module traffic (
input wire clk ,
input wire clr ,
output reg [5:0] lights
);
reg[2:0] state;
reg[3:0] count;

parameter S0 = 3'b000, S1 =3'b001, S2 = 3'b010, // states
          S3 = 3'b011, S4 = 3'b100, S5 = 3'b101;
parameter SEC5 = 4'b1111, SEC1 = 4'b0011; // delays

always @(posedge clk or posedge clr)
begin
  if (clr == 1)
    begin
      state <= S0;
      count <= 0;
    end
  else
    case(state)
      S0: if(count < SEC5)
        begin
          state <= S0;
          count <= count + 1;
        end
      else
        begin
          state <= S1;
          count <= 0;
        end
      S1: if(count < SEC1)
        begin
          state <= S1;
          count <= count + 1;
        end
      else
        begin
          state <= S2;
          count <= 0;
        end
      S2: if(count < SEC1)
        begin
          state <= S2;
          count <= count + 1;
        end
      else
        begin
          state <= S3;
          count <= 0;
        end
    end
end
```

Listing 8.6 (cont.) traffic.v

```
S3: if(count < SEC5)
    begin
        state <= S3;
        count <= count + 1;
    end
else
    begin
        state <= S4;
        count <= 0;
    end
S4: if(count < SEC1)
    begin
        state <= S4;
        count <= count + 1;
    end
else
    begin
        state <= S5;
        count <= 0;
    end
S5: if(count < SEC1)
    begin
        state <= S5;
        count <= count + 1;
    end
else
    begin
        state <= S0;
        count <= 0;
    end
    default state <= S0;
endcase
end

always @(*)
begin
    case(state)
        S0: lights = 6'b100001;
        S1: lights = 6'b100010;
        S2: lights = 6'b100100;
        S3: lights = 6'b001100;
        S4: lights = 6'b010100;
        S5: lights = 6'b100100;
        default lights = 6'b100001;
    endcase
end
endmodule
```

Listing 8.7 clkdiv.v

```
// Example 62b: clock divider
module clkdiv (
input wire clk ,
input wire clr ,
output wire clk3
);
reg [24:0] q;

// 25-bit counter
always @(posedge clk or posedge clr)
begin
if(clr == 1)
q <= 0;
else
q <= q + 1;
end

assign clk3 = q[24]; // 3 Hz

endmodule
```

Listing 8.8 traffic_lights_top.v

```
// Example 62: traffic_lights_top
module traffic_lights_top (
input wire clk ,
input wire [3:3] btn ,
output wire [7:2] ld
);
wire clk3;
wire clr;

assign clr = btn[3];

clkdiv U1 (.clk(clk),
.clr(clr),
.clk3(clk3)
);

traffic U2 (.clk(clk3),
.clr(clr),
.lights(ld)
);

endmodule
```